

## 1. Gantt chart

Display Week: 1

[illegible]

## Measurements

### a) Resistance

- i) Full light: 2.5k $\Omega$
- ii) ambient light: 12k $\Omega$
- iii) ambient dark: 1M $\Omega$
- iv) total darkness: 2.72M $\Omega$

### b) R<sub>motor</sub>: 6 $\Omega$

## R2

$$R2 = V_{out} / (V_{in} - V_{out}) * R1$$

- a) when V<sub>out</sub> is 2v (Dark, motor stopped) : 283k $\Omega$
- b) when V<sub>out</sub> is 8v (Light, motor working aggressively): 96k $\Omega$

## V<sub>out</sub>

$$V_{out} = R2 / (R1 + R2) * V_{in}$$

- a) when Dark (motor stopped): 2.0007v
- b) when Light (motor working): 8v

## Note:

- I believe this circuit and my prototype is working because it has worked perfectly on my breadboard. I just need to tune more to get it accustomed with the demonstration environment which is with dark light. I also have to measure the resistances again to gain more accurate R2 values.
- Sometimes, debugging was needed on my breadboard so that's why neatly designed circuit is an important thing to consider.
- For excitatory, 10k $\Omega$  was enough to operate the motor. But for inhibitory operation, 1M $\Omega$  was needed. I have to figure why.